

# Chapter 28: Circuits

28-1

See sections 1-8

An EMF device = a charge pump - a battery, solar cell, fuel cell, etc, that pushes charge carriers thru a circuit

$$\mathcal{E} = \frac{dW}{dq} = \text{The emf of a device}$$

= work  $dW$  done by the emf device (often a battery) at it pushes charge  $dq$  thru circuit

$\mathcal{E}$  has units of energy/charge, or  $J/C = 1 \text{ volt}$  in SI units


Example: a battery with a potential difference of 9 volts across its terminals has an emf of  $\mathcal{E} = 9 \text{ v}$ .

The power of an emf device is

$$\mathcal{E} = \frac{dW}{dq} = \frac{dW/dt}{dq/dt} = \frac{P}{i}$$

so  $P = i\mathcal{E}$  = rate at which the emf device does work on the charge carriers.

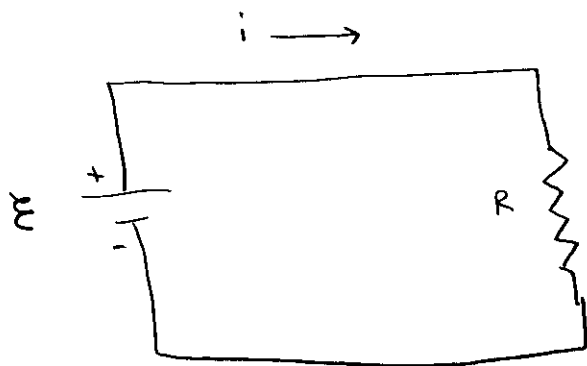Consider this simple circuit: an emf device (ie, a battery) hooked up to a resistor  $R$ :



Since  $dW = \epsilon dq =$  small work done by battery on small charge  $dq$  as it is pushed thru the circuit

but that energy deposited at  $dq$  gets dissipated in the resistor  $R$  at the rate  $P = i^2 R$  (27-22)


$$\text{so } dW = \epsilon dq = P dt = i^2 R dt$$

$$\text{so } \underbrace{\epsilon \frac{dq}{dt}}_{i = \text{current}} = i^2 R$$

$$\Rightarrow i = \frac{\epsilon}{R} = \text{current thru this circuit}$$

Kirchoff's voltage law.

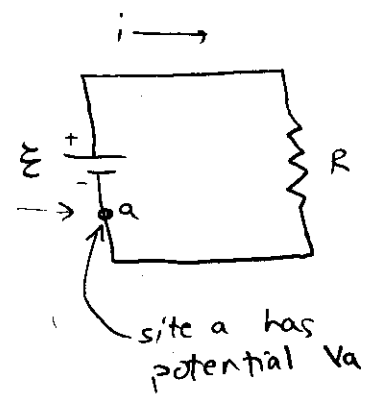Mentally walk thru the circuit in the clockwise direction, starting at a. Keep track of all changes in the circuit's potential,  $V$ .



When you again return to site a, the potential should be unchanged.

⇒ This is Kirchoff's voltage law: The sum of all changes in potential  $V$  about any loop in a circuit is zero.

Apply Kirchoff's Law to this circuit, starting at a, and travelling in the direction of the current flow

$$V_a + \epsilon - iR = V_a$$

← back to where we began

initial potential

↑

potential increase as you cross the battery towards the + terminal

↑

potential drop as you cross R in the direction of the current flow

←

⇒  $i = \frac{\epsilon}{R}$  = current thru circuit, as expected.


Note - you can travel in the direction opposite to the current.

In this case,  $\mathcal{E} \rightarrow -\mathcal{E}$   
and  $-iR \rightarrow +iR$  } because the potential differences reverse as you travel in the opposite direction

The result is the same:  $i = \frac{\mathcal{E}}{R}$
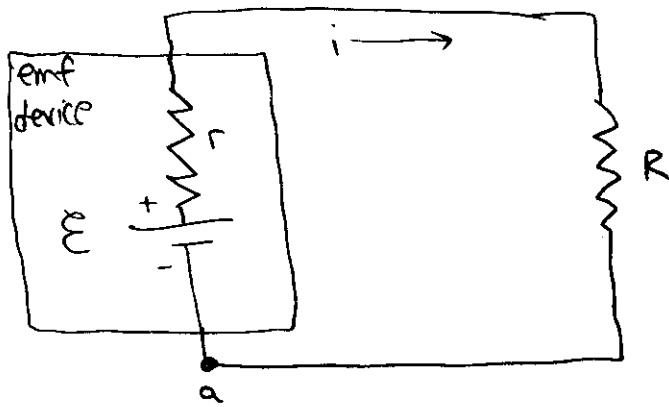
### Internal Resistance:

Most emf devices also have some internal resistance  $r$ :



Start at  $a$  and use the Kirchhoff voltage law, clockwise:

$$V_a + \mathcal{E} - ir - iR = V_a$$


$$\Rightarrow \mathcal{E} = i(r+R)$$

$$= iR_{eq} \quad \text{where } R_{eq} = r+R \\ = \text{equivalent resistance}$$

$$\text{so } i = \frac{\mathcal{E}}{R_{eq}} = \frac{\mathcal{E}}{r+R} = \text{current thru circuit.}$$

Note that we can replace the two resistors  $r$  and  $R$  with an equivalent resistor  $R_{eq} = r + R$

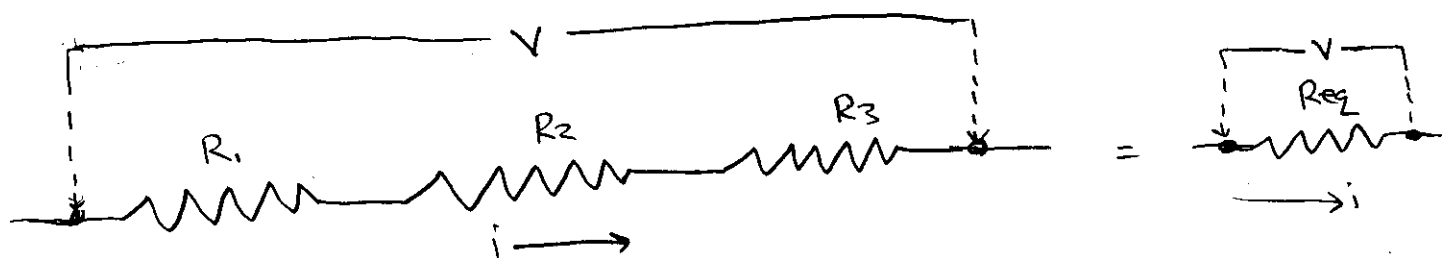Resistors in series (ie, one after the other) :




These resistors have an equivalent resistance

$$R_{eq} = \sum_{j=1}^n R_j = R_1 + R_2 + R_3 + \dots$$


Both sets of resistors will have the same voltage  $V$  across them, and the same current  $i$  running thru them.

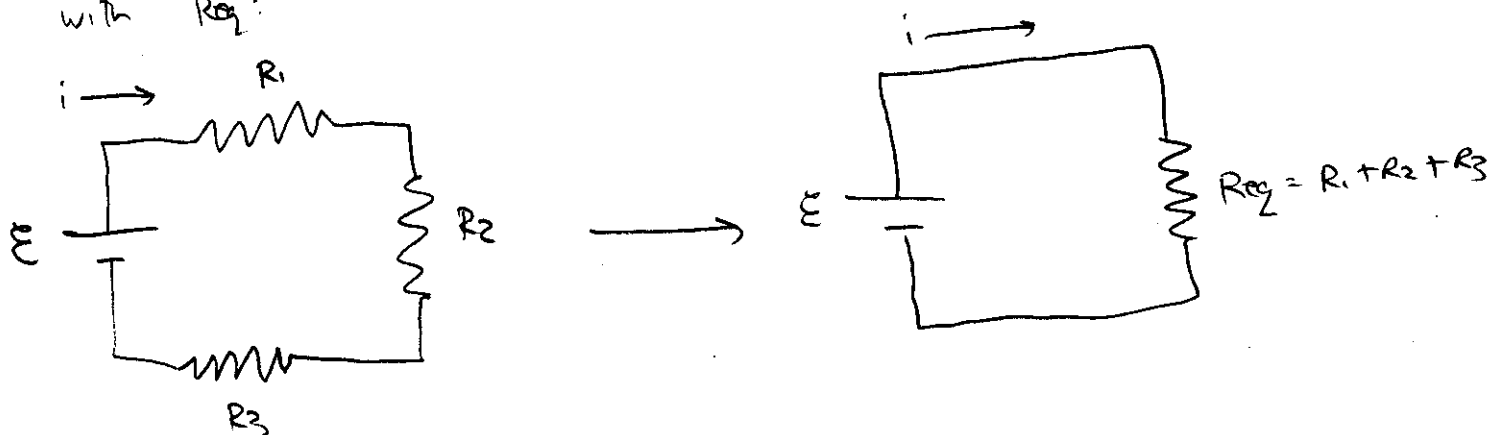When analyzing circuits, simplify by replacing  $R_1, R_2, etc$  with  $R_{eq}$ :


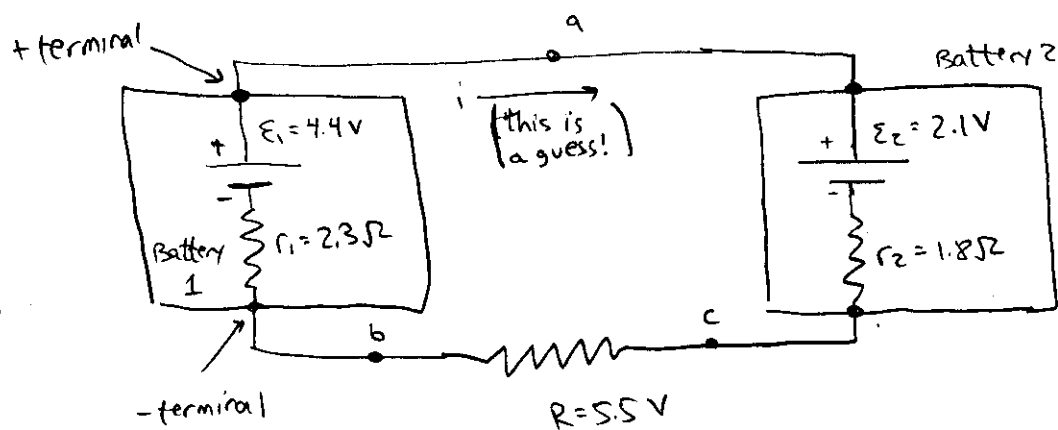
## Sample Problem 28-1

a.) what is the current thru this circuit?



Note that the batteries are connected + to +!  
 $\Rightarrow$  the emf of one battery is going to oppose the other!  
 (actually, one battery will tend to charge up the other)

Use Kirchhoff's voltage law, start at a, and travel counterclockwise, against the assumed current:

$$V_a - \mathcal{E}_1 + ir_1 + iR + ir_2 + \mathcal{E}_2 = V_a$$

$$\text{so } i(r_1 + R + r_2) = \mathcal{E}_1 - \mathcal{E}_2$$

$$\text{or } i = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_{\text{eq}}} \quad \text{where } R_{\text{eq}} = r_1 + R + r_2 = 9.6\Omega$$

$$= \frac{2.3\text{V}}{9.6\Omega}$$

so  $i = 0.24$  amps = current thru circuit.

which way is this current flowing? clockwise or counter-clockwise?

b.) What is the potential difference across the terminals of battery 1?

That difference is  $V_a - V_b$ .

(Note that resistor  $r_1$  is internal to the battery's terminals.)

Again use K's voltage law.

This time, start at b, and go clockwise:

$$V_b - ir_1 + \mathcal{E}_1 = V_a$$


$$\begin{aligned} \text{so } V_a - V_b &= -ir_1 + \mathcal{E}_1 = 3.85 \text{ volts} \\ &= \text{voltage across terminals} \\ &\quad \text{in battery 1} \end{aligned}$$

Note that  $V_a - V_b$  is slightly less than  $\mathcal{E}_1$  due to the battery's internal resistance  $r_1$ .

## Multi-loop Circuits


Kirchoff's current law: The sum of all currents entering a junction = sum of all exiting currents

example

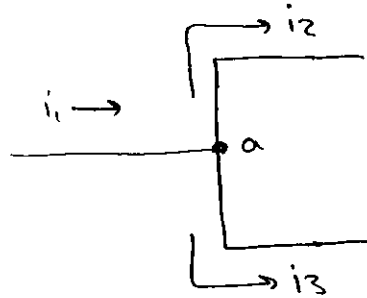

$$i_1 = i_2 + i_3$$

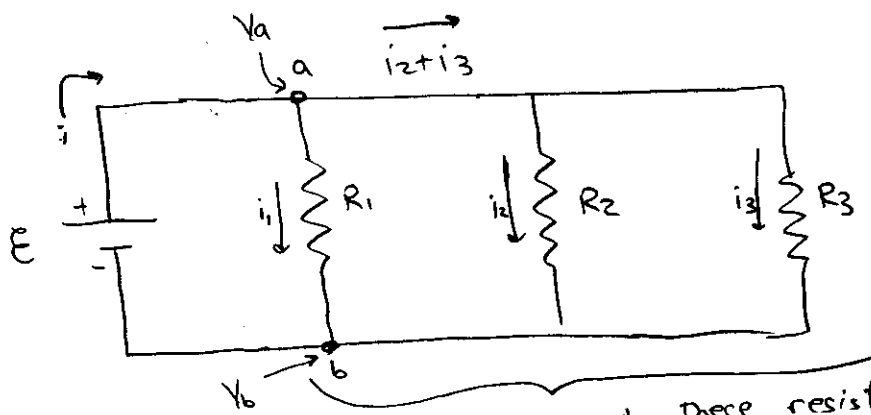Use this result to examine a multi loop circuit.



Note that these resistors are in "parallel"

$\Rightarrow$  all resistors in parallel have the same potential difference across them,  $V_b - V_a \equiv V$

However, the currents thru these resistors differ:

$$i_1 = \frac{V}{R_1}$$

$$i_2 = \frac{V}{R_2}$$

$$i_3 = \frac{V}{R_3}$$



Kirchoff's current law at site a says:


$$i = i_1 + i_2 + i_3 = v \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

replace with  $\frac{1}{R_{eq}}$

⇒ the equivalent resistance for resistors in parallel is

$$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

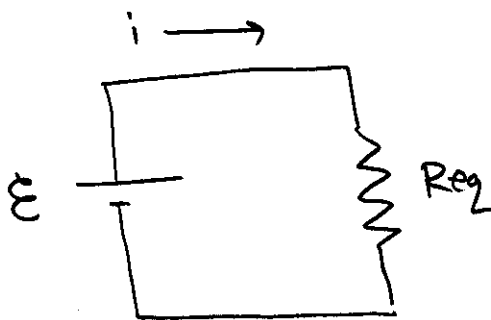
So we can replace our multi-loop circuit with the simpler circuit



Use this trick to simplify your analysis of circuits.



In Summary :

For resistors in series:

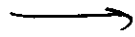

$$R_{eq} = R_1 + R_2 + R_3$$




For resistors in parallel

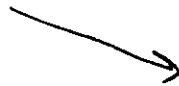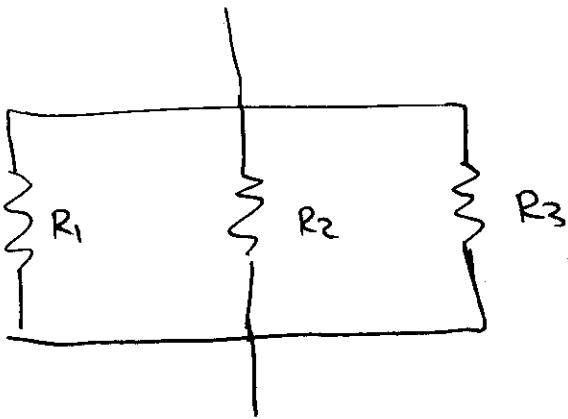

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



What about capacitors? See Section 26-4:

For C's in series:

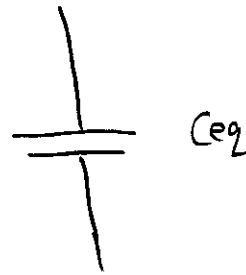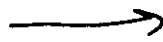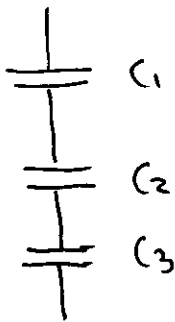

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$


For C's in parallel:

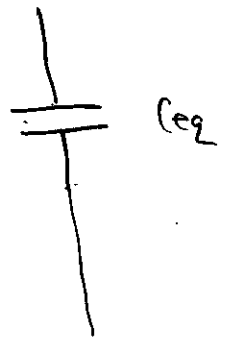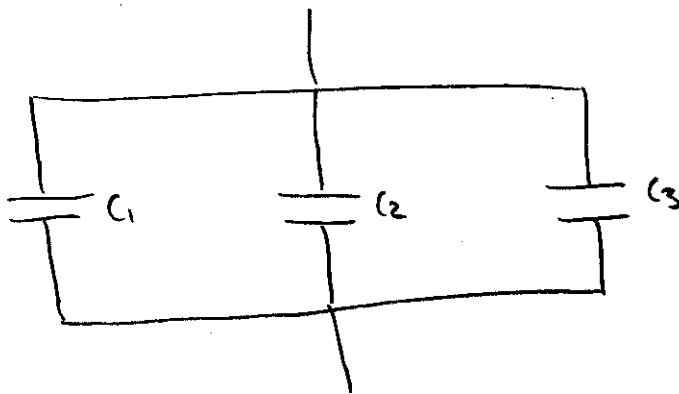

where  $C_{eq} = C_1 + C_2 + C_3$

# RC Circuits

Let's examine this RC circuit:

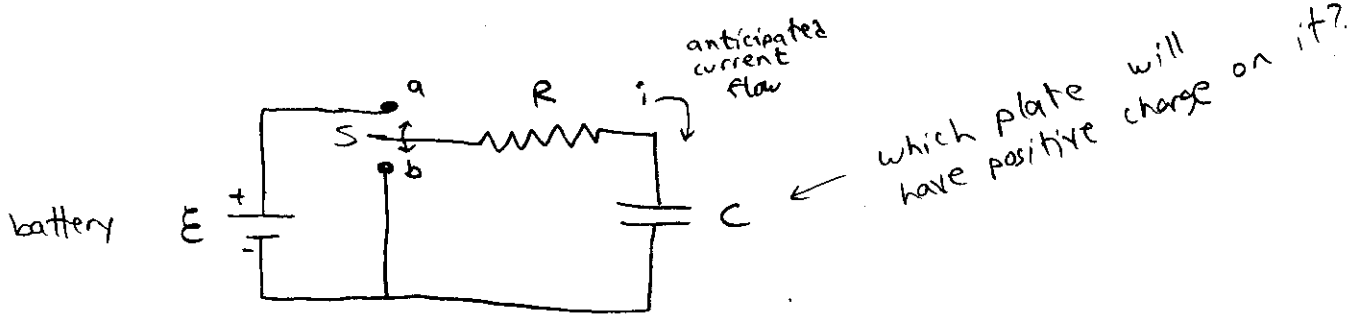

Note: closing the switch S at point a completes the circuit. current will flow, and charge up C.

Then, closing the switch at point b completes another circuit. This discharges the capacitor.

1. charge the capacitor (ie, close switch on a).  
Kirchoff's law (starting at - terminal, running clockwise):

$$\mathcal{E} - iR - \frac{q}{C} = 0$$

↑ recall that

$$V = \frac{q}{C} = \text{potential across } C$$

minus sign indicates that the potential decreases

as you travel from + plate to - plate:

$$\left. \begin{array}{c} + \\ \hline - \end{array} \right\} \Delta V = -\frac{q}{C}$$

Since  $i = \frac{dq}{dt}$ ,

$$R \frac{dq}{dt} + \frac{q}{C} = \mathcal{E} \leftarrow \text{differential eqn' for charge } q(t) \text{ on capacitor}$$

solution:  $q(t) = C\mathcal{E}(1 - e^{-t/RC})$

verify:  $\frac{dq}{dt} = + \frac{C\mathcal{E}}{RC} e^{-t/RC}$

so  $R \frac{dq}{dt} + \frac{q}{C} = \mathcal{E} e^{-t/RC} + \mathcal{E}(1 - e^{-t/RC}) = \mathcal{E} \checkmark$

Also, the current that charges the capacitor is



$$i = \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$$

while the voltage  $V_c$  across the capacitor is

$$V_c = \frac{q}{C} = \mathcal{E}(1 - e^{-t/RC})$$

Note that the product  $RC = \text{time-constant } \tau$

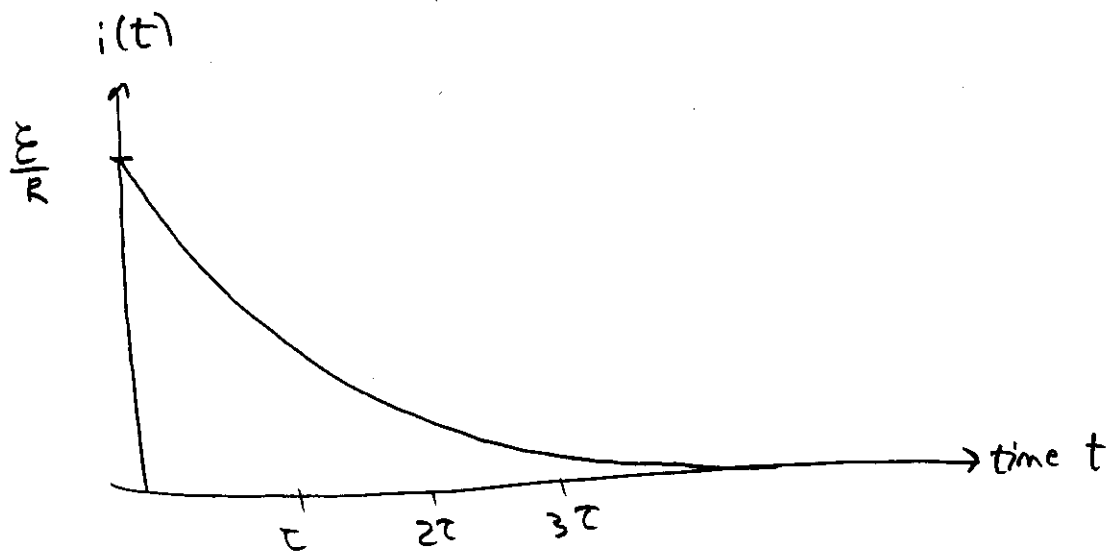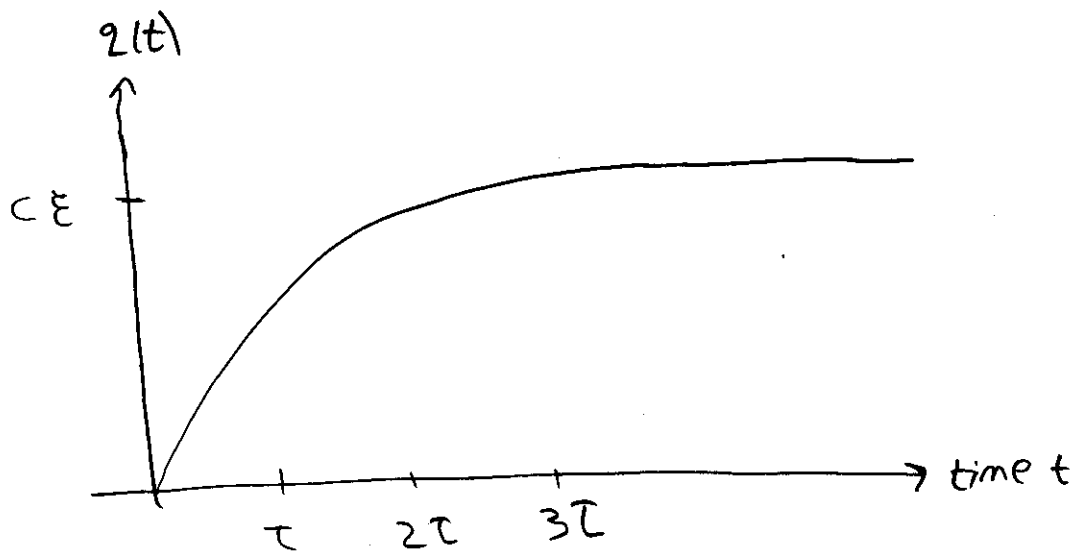$\tau = RC = \text{e-folding time} = \text{time to increase } q(t)$   
by a factor  $e' = 2.72 \dots$



2. To discharge the capacitor:

put switch in position b.

This effectively removes the battery,  $\mathcal{E}$

The equation for this circuit is obtained

by setting  $\mathcal{E} = 0$ :

$$R \frac{dq}{dt} + \frac{q}{C} = 0$$

$$\text{or } \frac{dq}{dt} = - \frac{q}{\tau}$$

which has solution

$$q(t) = q_0 e^{-t/\tau}$$

What is  $q_0$ ?

$q_0$ : charge on fully charged C  
=  $C\mathcal{E}$

The current is

$$i(t) = \frac{dq}{dt} = - \frac{q_0}{\tau} e^{-t/\tau}$$

$$= - \frac{q_0}{RC} e^{-t/\tau}$$

$\Rightarrow$  discharging C also occurs  
over an exponential timescale  $\tau = RC$